

Computer Organization

Lecture 10 - Multiplication and Division

Reading: 3.3-3.4

Outline - Multiplication and Division

- ▶ **Multiplication**

- ▶ **Review: Shift & Add Multiplication**



- ▶ **Review: Booth's Algorithm**

- ▶ **Combinational Multiplication**


- ▶ **MIPS Multiplication Instructions**

- ▶ **Division**

- ▶ **Summary**

Multiplication

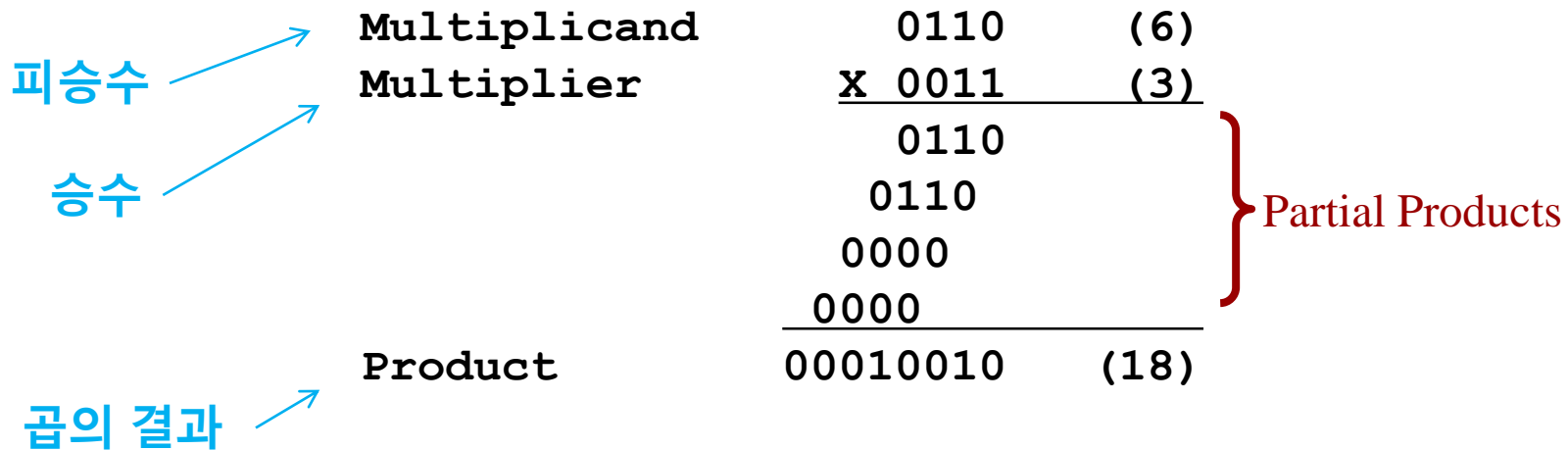- ▶ Basic algorithm analogous to decimal multiplication
 - ▶ Break multiplier into digits
 - ▶ Multiply one digit at a time;
shift multiplicand to form partial products
 - ▶ Create product as sum of partial products




- ▶ **n** bit multiplicand X **m** bit multiplier = (**n+m**) bit product


Animation - 1st Cut Multiplier

Multiplicand의 자릿수를 하나씩 올리면서 (shift left) 연산한다.

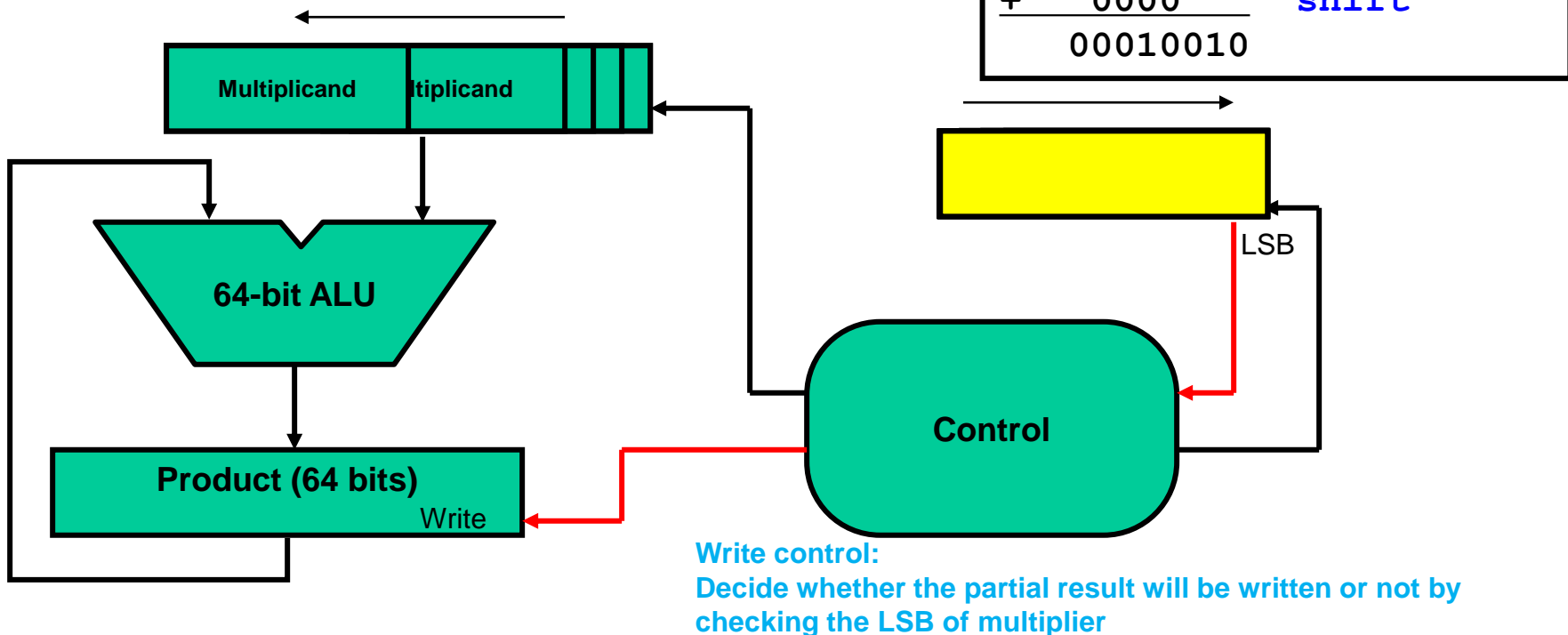- ▶ **Multiplicand** shifts left
- ▶ Multiplier shifts right
- ▶ Sample LSB of multiplier to decide whether to add



Algorithm - 1st Cut Multiplier

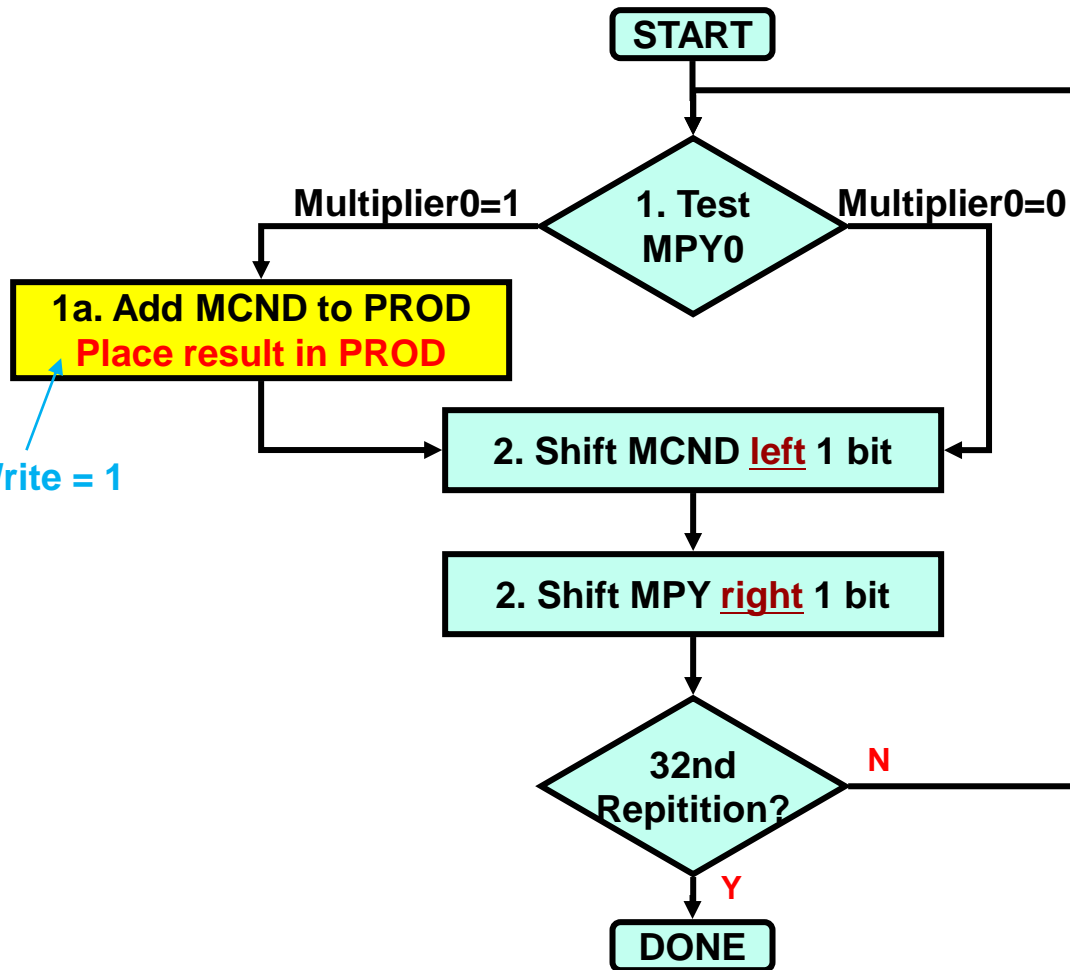


	0110	
x	0011	
+	0110	add + shift
+	0110	add + shift
+	0000	shift
+	0000	shift
	00010010	

Sequential Multiplier - 2nd Version


연산을 하고 나서 product의 자릿수를
하나씩 내린다 (shift right) .

- ▶ Observation: we're only adding 32 bits at a time
- ▶ Clever idea: Why not...
 - ▶ Hold the multiplicand still and...
 - ▶ **Shift the product right!**

0110	(6)
x 0011	(3)
<hr/>	
00000000	current product
00110000	add & shift rht
01001000	add & shift rht
00100100	no add & shift rht
00010010	no add & shift rht

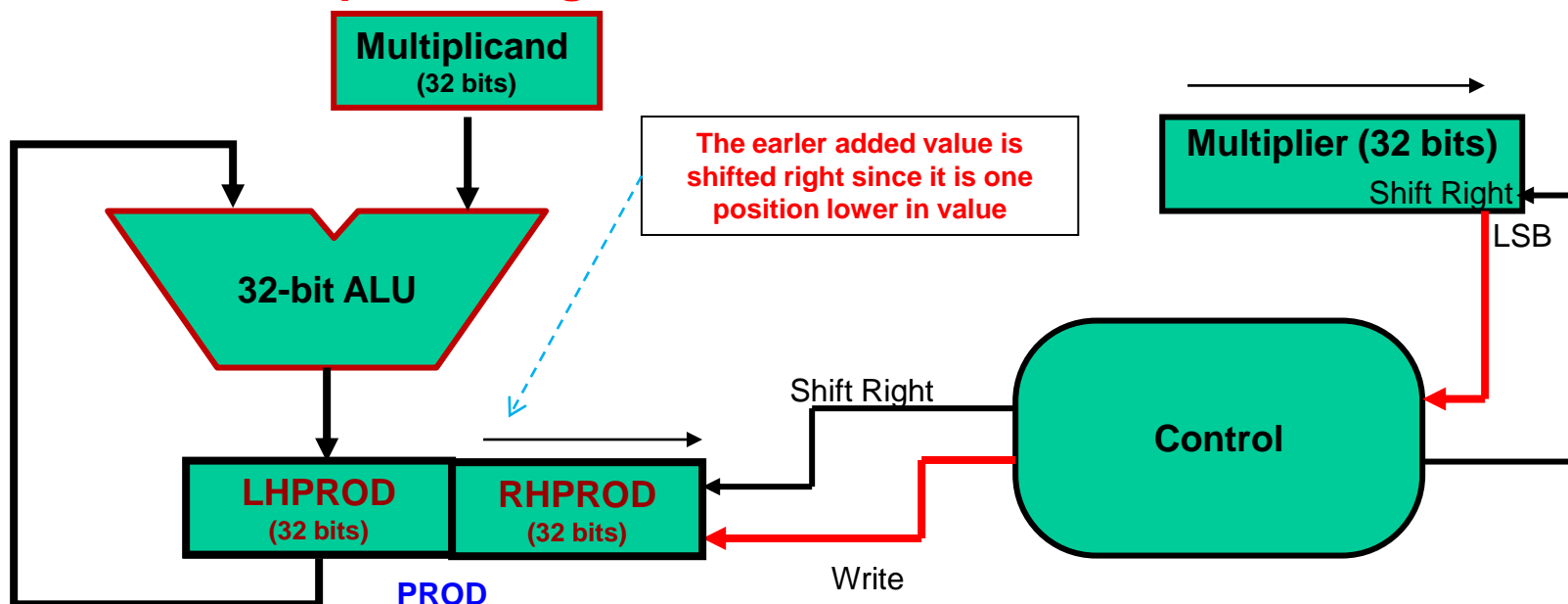


Algorithm - 2nd Version Multiplier

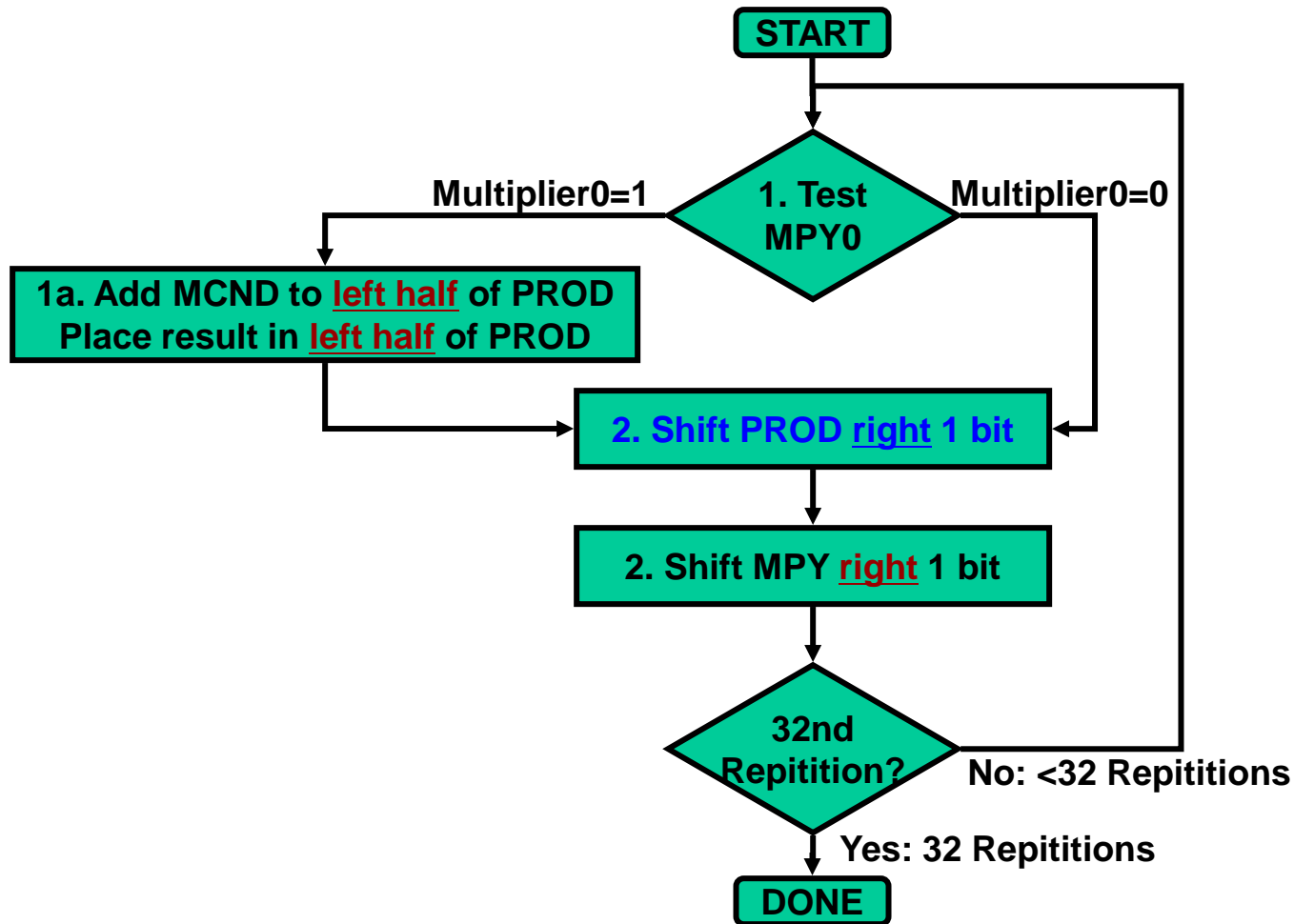


Sequential Multiplier - 3rd Version

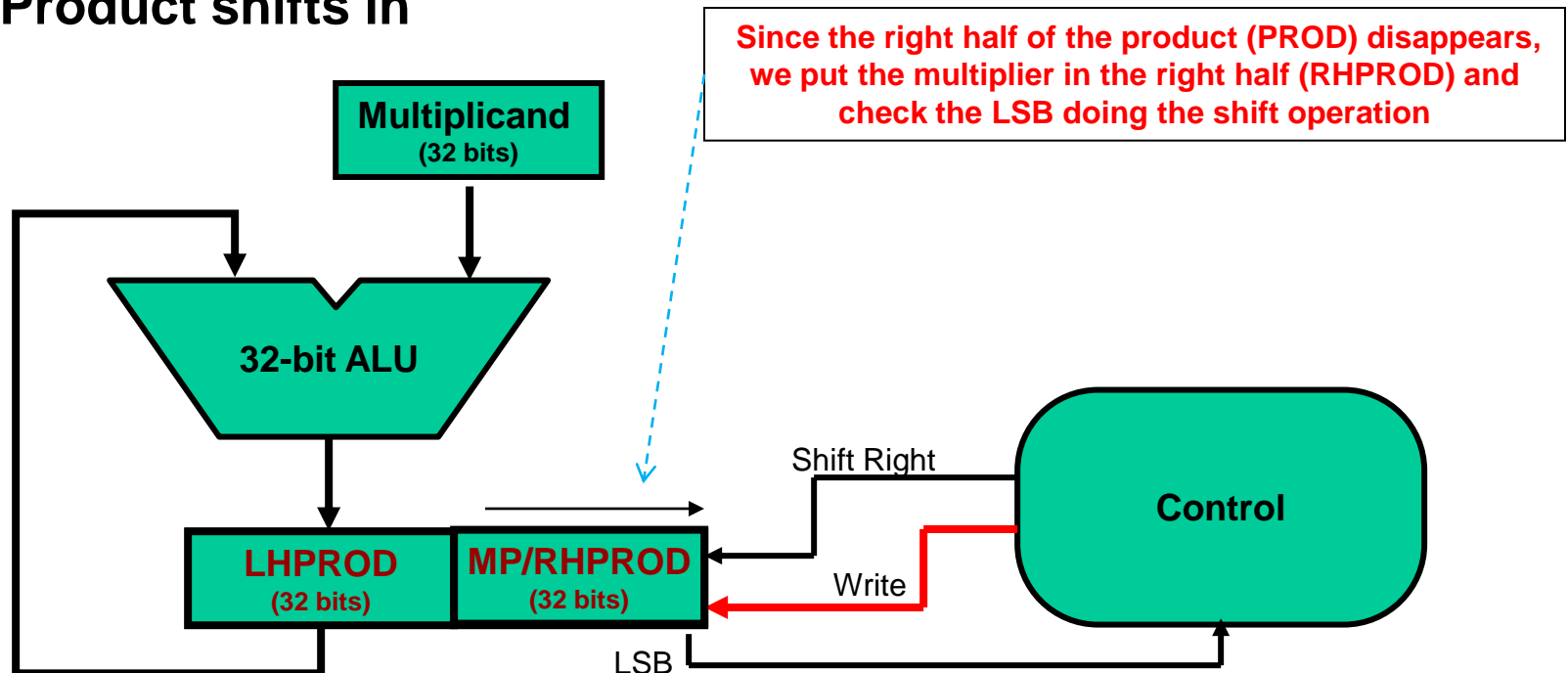- ▶ Observation: we can store **the multiplier and product** in the same register!
 - ▶ As multiplier **shifts out**....
 - ▶ Product shifts in



Algorithm - 3rd Version Multiplier

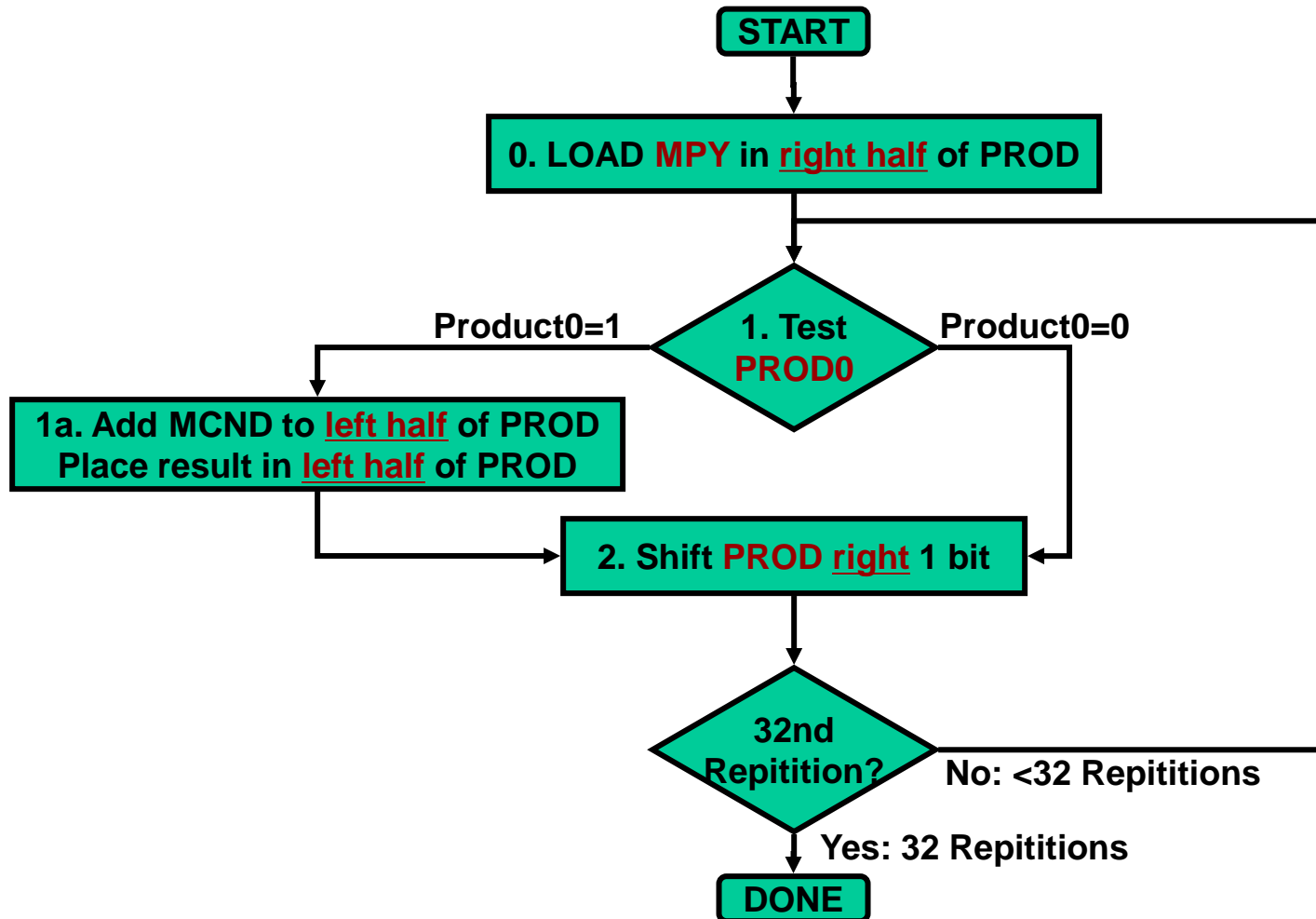

Outline - Multiplication and Division

- ▶ **Multiplication**
 - ▶ Review: Shift & Add Multiplication
 - ▶ Review: Booth's Algorithm ◀
 - ▶ Combinational Multiplication
 - ▶ MIPS Multiplication Instructions
- ▶ Division
- ▶ Summary

Signed Multiplication with Booth's Algorithm

- ▶ Originally proposed to reduce **addition steps**
- ▶ Bonus: works for two's complement numbers
- ▶ Uses shifting, addition, and subtraction

Booth's Algorithm

- ▶ Observation: if we can both add and subtract, there are multiple ways to create a product
- ▶ Example: multiply 2_{ten} by 6_{ten} ($0010_{\text{two}} \times 0110_{\text{two}}$)
 - ▶ $2 \times 6 = 2 \times (2 + 4) = (2 \times 2) + (2 \times 4)$ OR
 - ▶ $2 \times 6 = 2 \times (-2 + 8) = (2 \times -2) + (2 \times 8)$

Regular Algorithm

	0010	
x	0110	
+	0000	shift
+	0010	add + shift
+	0010	add + shift
+	0000	shift
	00001100	

Booth's Algorithm

	0010	
x	0110	(= 1000 - 0010)
	0000	shift
-	0010	sub + shift
	0000	shift
+	0010	add + shift
	00001100	

Booth's Algorithm Continued

▶ Question:

- ▶ How do we know when to subtract?
- ▶ When do we know when to add?

▶ Answer: look for “runs of 1s” in multiplier

▶ Example: 001110011

▶ Working from Right to Left, any “run of 1’s” is equal to:

- value of first digit that’s one
- +value of first digit that’s zero


▶ Example : 001110011

- First run: $-1 + 4 = 3$
- Second run: $-16 + 128 = 112$
- Total: $(-1 + 4) + (-16 + 128) = 3 + 112 = 115$

Implementing Booth's Algorithm

- ▶ Scan multiplier bits from right to left
- ▶ Recognize the **beginning** and **in** of a run looking at only 2 bits at a time

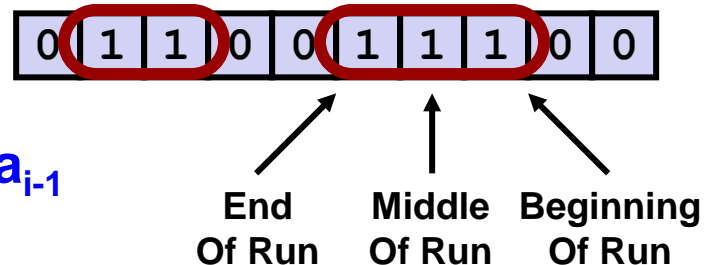
- ▶ “Current” bit: a_i
- ▶ Bit to right of “current” bit: a_{i-1}



Bit a_i	Bit a_{i-1}	Explanation
1	0	Begin Run of 1's
1	1	Middle of Run of 1's
0	1	End of Run
0	0	Middle of Run of 0's

Implementing Booth's Algorithm

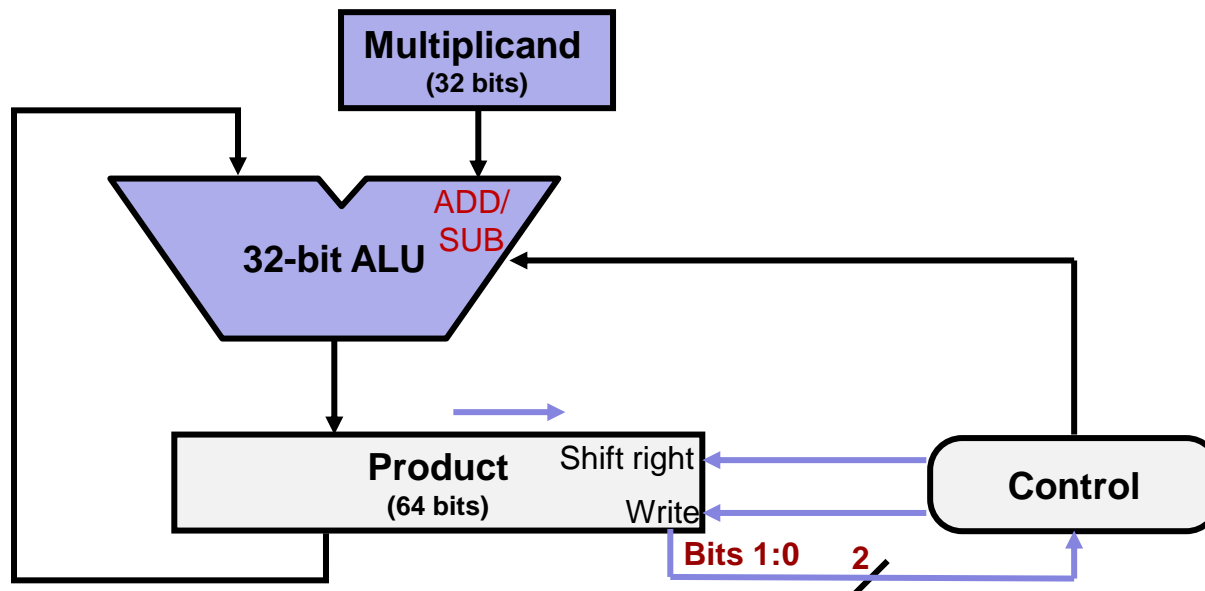- ▶ Key idea: test 2 bits of **multiplier** at once
 - ▶ 10 - subtract (beginning of run of 1's)
 - ▶ 01 - add (end of run of 1's)
 - ▶ 00, 11 - do nothing (middle of run of 0's or 1's)



Booth's Algorithm Example

Multiply 4 X -9

00100

x 10111

Remember

4 = 000100

-4 = 111100

-9

<pre> 000000101110 +111100 ----- 111100101110 111110010111 111111001011 111111100101 +000100 ----- 000011100101 000001110010 +111100 ----- 111101110010 111110111001 </pre>	<p>(sub 4 / add -4)</p> <p>(shift after add)</p> <p>(shift w/ no add)</p> <p>(shift w/ no add)</p> <p>(add +4)</p> <p>(shift after add)</p> <p>(sub 4 / add -4)</p> <p>(shift after add)</p>
<p>Drop leftmost & rightmost bit</p>	
<p>1111011100 = -(0000100011 + 1)</p> <p style="margin-left: 100px;">= -(0000100100)</p> <p style="margin-left: 100px;">= -36 = 4 x -9!</p>	

Outline - Multiplication and Division

- ▶ **Multiplication**
 - ▶ Review: Shift & Add Multiplication
 - ▶ Review: Booth's Algorithm
 - ▶ **Combinational Multiplication** ◀
 - ▶ MIPS Multiplication Instructions
- ▶ **Division**
- ▶ **Summary**


Combinational Multipliers

- ▶ **Goal: make multiplication faster**
- ▶ **General approach**
 - ▶ Use AND gates to generate partial products
 - ▶ Sum partial products with adders

Array Multiplier


$$\begin{array}{r}
 X_3 X_2 X_1 X_0 \\
 \times Y_3 Y_2 Y_1 Y_0 \\
 \hline
 Z_7 Z_6 Z_5 Z_4 Z_3 Z_2 Z_1 Z_0
 \end{array}$$

X = multiplicand
Y = multiplier

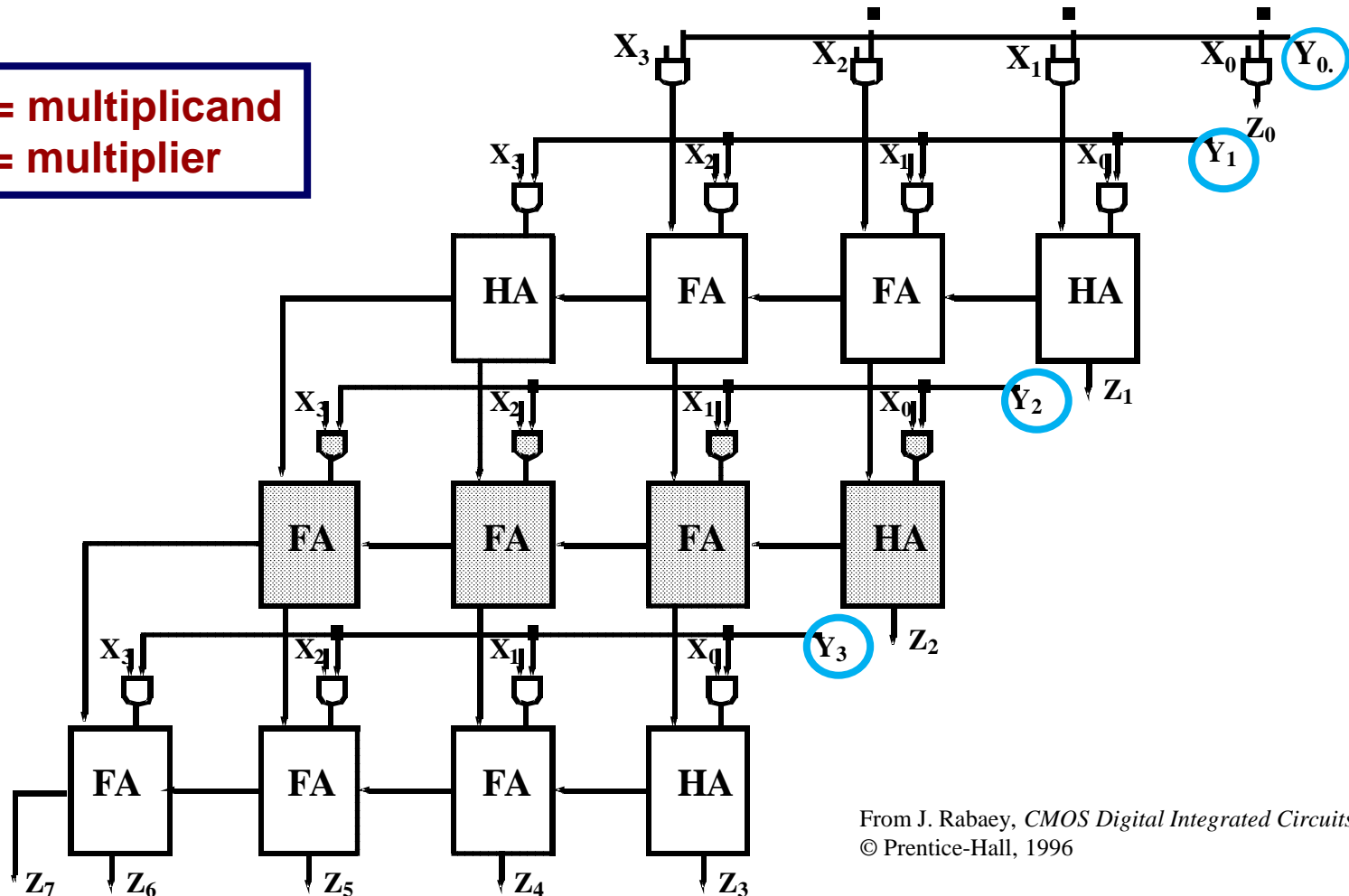

From J. Rabaey, *CMOS Digital Integrated Circuits*
© Prentice-Hall, 1996

Array Multiplier - Critical Paths

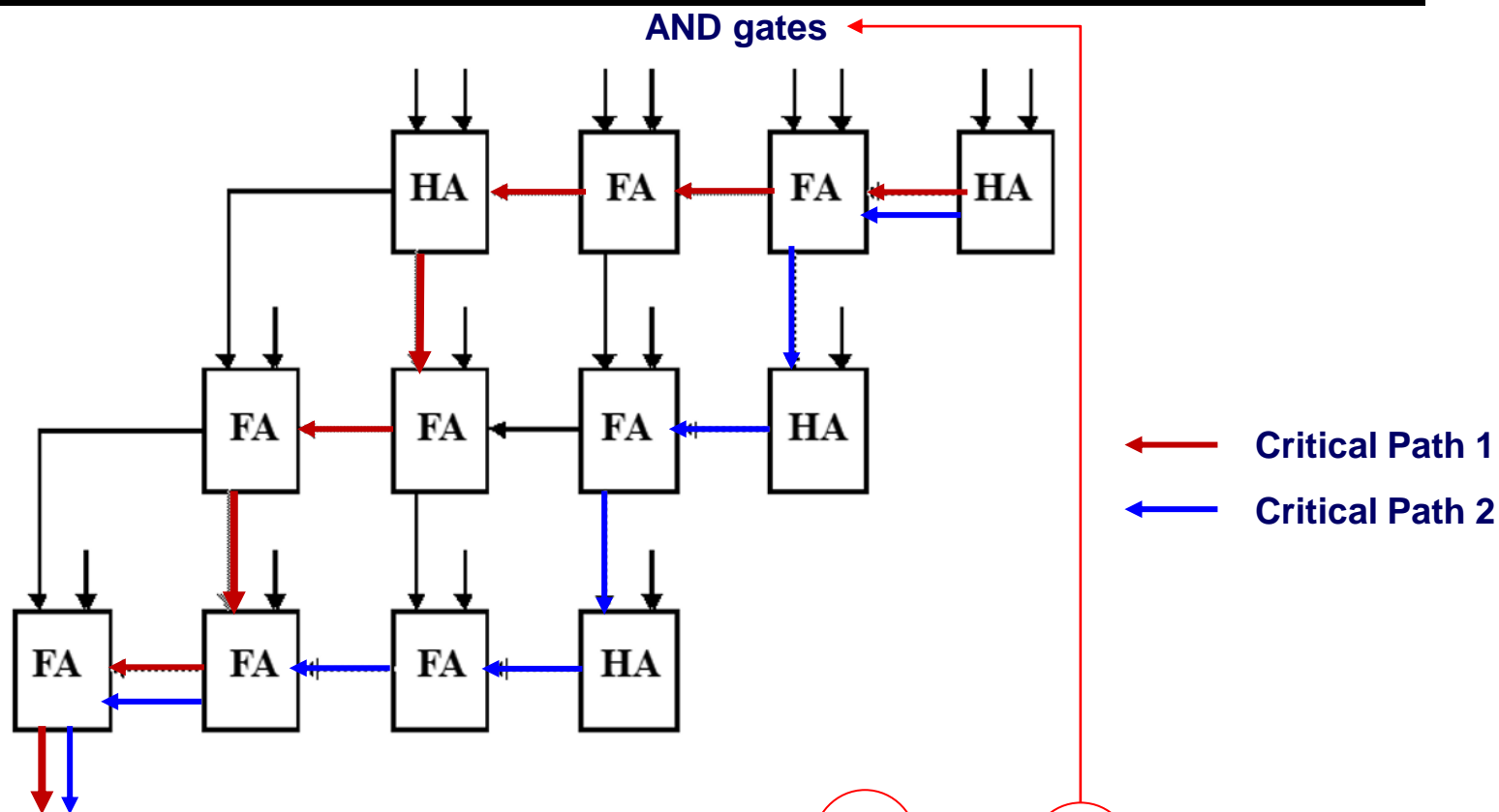

$$T_{mult} \approx [(M-1)+(N-2)]t_{carry} + (N-1)t_{sum} + t_{and}$$

From J. Rabaey, *CMOS Digital Integrated Circuits*
© Prentice-Hall, 1996

Outline - Multiplication and Division

- ▶ **Multiplication**

- ▶ Review: Shift & Add Multiplication
- ▶ Review: Booth's Algorithm
- ▶ Combinational Multiplication
- ▶ **MIPS Multiplication Instructions** ◀

- ▶ **Division**

- ▶ **Summary**

Multiply Instructions in MIPS

- ▶ **MIPS adds new registers for product result:**
 - ▶ **Hi** - upper 32 bits of product
 - ▶ **Lo** - lower 32 bits of product
- ▶ **MIPS multiply instructions**
 - ▶ `mult $s0, $s1`
 - ▶ `multu $s0, $s1`
- ▶ **Accessing Hi, Lo registers**
 - ▶ `mfhi $s1`
 - ▶ `mflo $s1`


Outline - Multiplication and Division

- ▶ **Multiplication**
 - ▶ Review: Shift & Add Multiplication
 - ▶ Review: Booth's Algorithm
 - ▶ Combinational Multiplication
 - ▶ MIPS Multiplication Instructions
- ▶ **Division**
 - ▶ **Division Algorithms** ◀
 - ▶ MIPS Division Instructions
- ▶ **Summary**

Division Overview


1st version H/W => next page

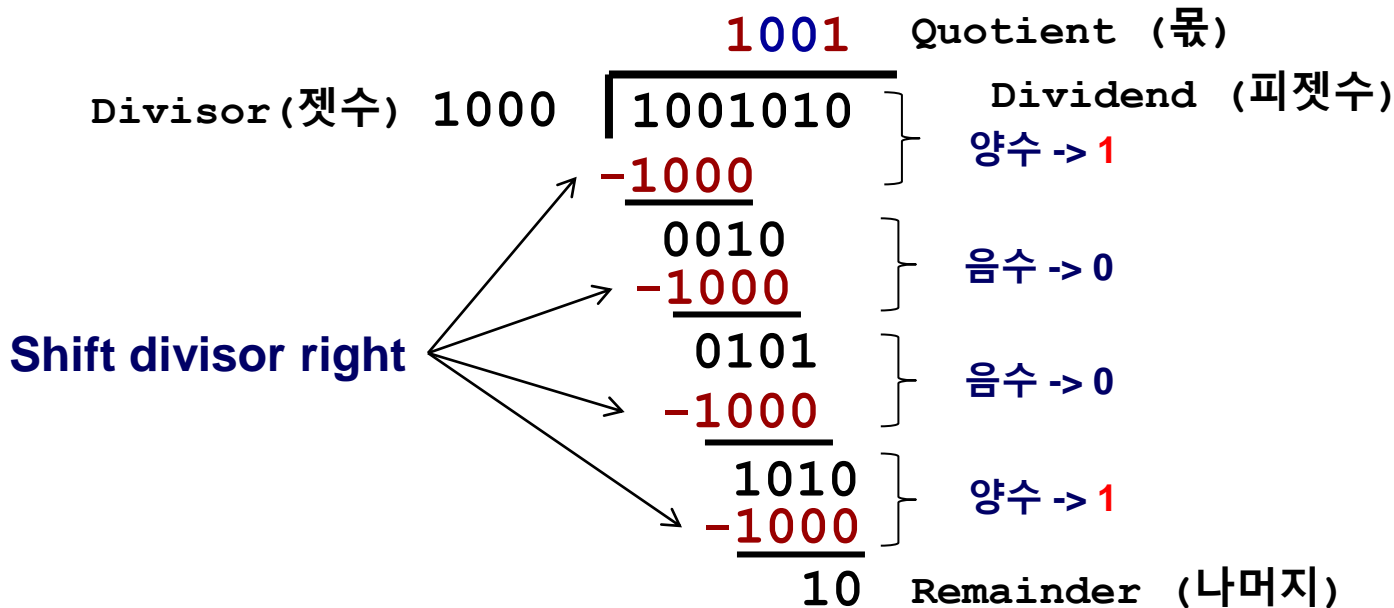- ▶ Grammar school algorithm: long division
 - ▶ Subtract shifted divisor from dividend when it “fits”
 - ▶ Quotient bit: 1 or 0
- ▶ Question: how can hardware tell “when it fits?”



$$\text{Dividend} = \text{Quotient} \times \text{Divisor} + \text{Remainder}$$


Computation Process

- ▶ $1001010/1000 = ?$
- ▶ $1001010 - \underline{1000000} = 0001010 \quad \Rightarrow Q = 0001$

- ▶ $0001010 - \underline{0100000} = \text{Neg (recover)} \quad \Rightarrow Q = 0010$
- ▶ $0001010 - \underline{0010000} = \text{Neg (recover)} \quad \Rightarrow Q = 0100$
- ▶ $0001010 - \underline{0001000} = 0000010 \quad \Rightarrow Q = 1001$
 - ▶ $Q = 1001, R = 0000010$
- ▶ Number of iterations = 4


Division Hardware - 1st Version

- ▶ Shift register moves divisor (DVR) to right
- ▶ ALU subtracts DVR, then restores (adds back) if $REM < 0$ (i.e. divisor was “too big”)

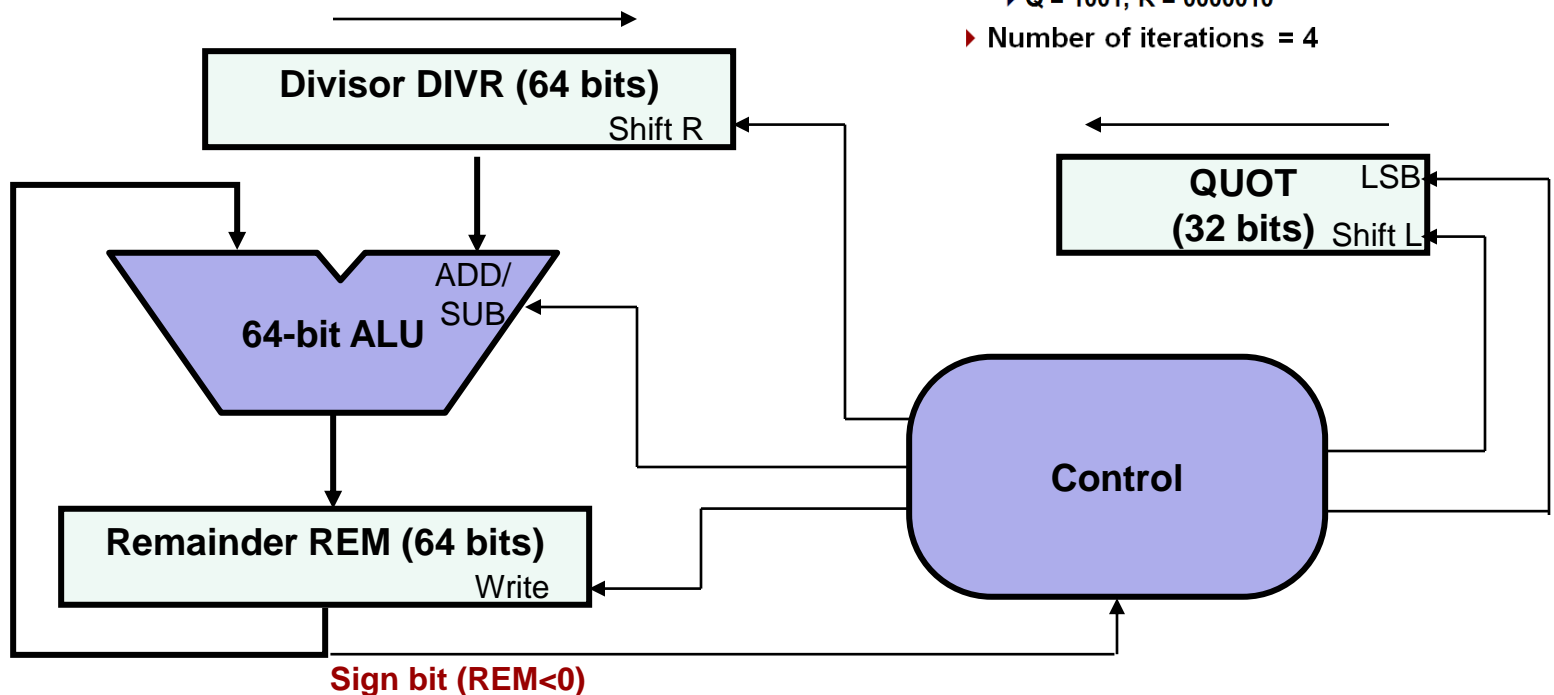- ▶ $1001010/1000 = ?$
- ▶ $1001010 - 1000000 = 0001010 \Rightarrow Q = 0001$
- ▶ $0001010 - 0100000 = \text{음수 (recover)} \Rightarrow Q = 0010$
- ▶ $0001010 - 0010000 = \text{음수 (recover)} \Rightarrow Q = 0100$
- ▶ $0001010 - 0001000 = 0000010 \Rightarrow Q = 1001$
 ▶ $Q = 1001, R = 0000010$
- ▶ Number of iterations = 4



Division Algorithm - First Version

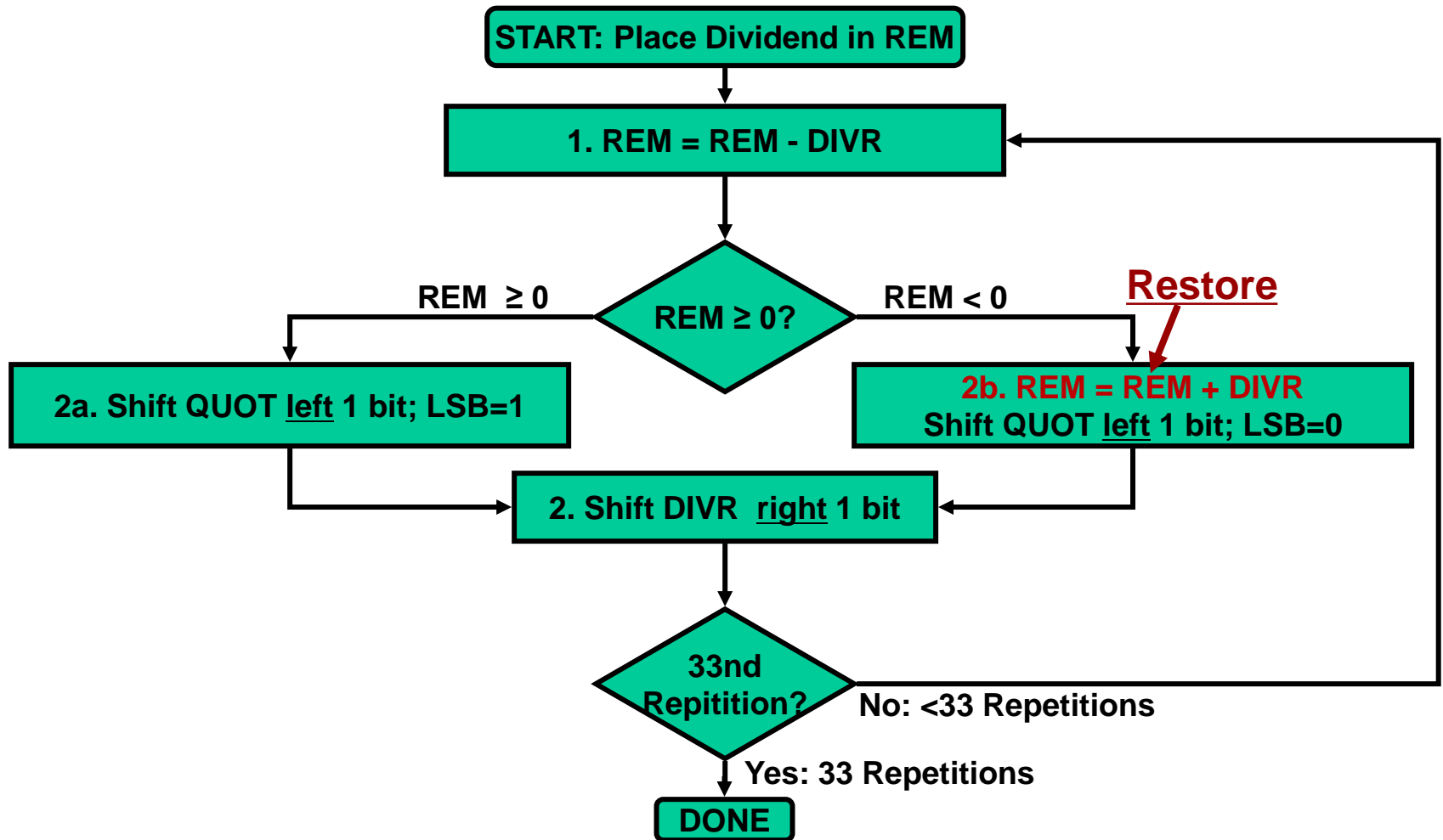

Divide 1st Version - Observations

- ▶ We only subtract 32 bits in each iteration
 - ▶ Idea: Instead of shifting divisor to right, **shift remainder to left**
- ▶ First step cannot produce a 1 in quotient bit
 - ▶ Switch order to **shift first, then subtract**
 - ▶ Save 1 iteration

Computation Process

▶ 10010100/00001000 = ?

subtract

First step: Always negative, so switch the order to shift first, then subtract => To save one iteration

▶ ~~0000000010010100 - 00001000 = Neg (recover) => Q = 00000000~~

▶ 0000000100101000 - 00001000 = Neg (recover) => Q = 00000000

▶ 0000001001010000 - 00001000 = Neg (recover) => Q = 00000000

▶ 0000010010100000 - 00001000 = Neg (recover) => Q = 00000000

▶ 0000100101000000 - 00001000 = Pos => Q = 00000001

▶ 0000001010000000 - 00001000 = Neg (recover) => Q = 00000010

▶ 0000010100000000 - 00001000 = Neg (recover) => Q = 00000100


▶ 0000101000000000 - 00001000 = Pos => Q = 00001001

▶ 0000010000000000

remainder


Divide Hardware - 2nd Version

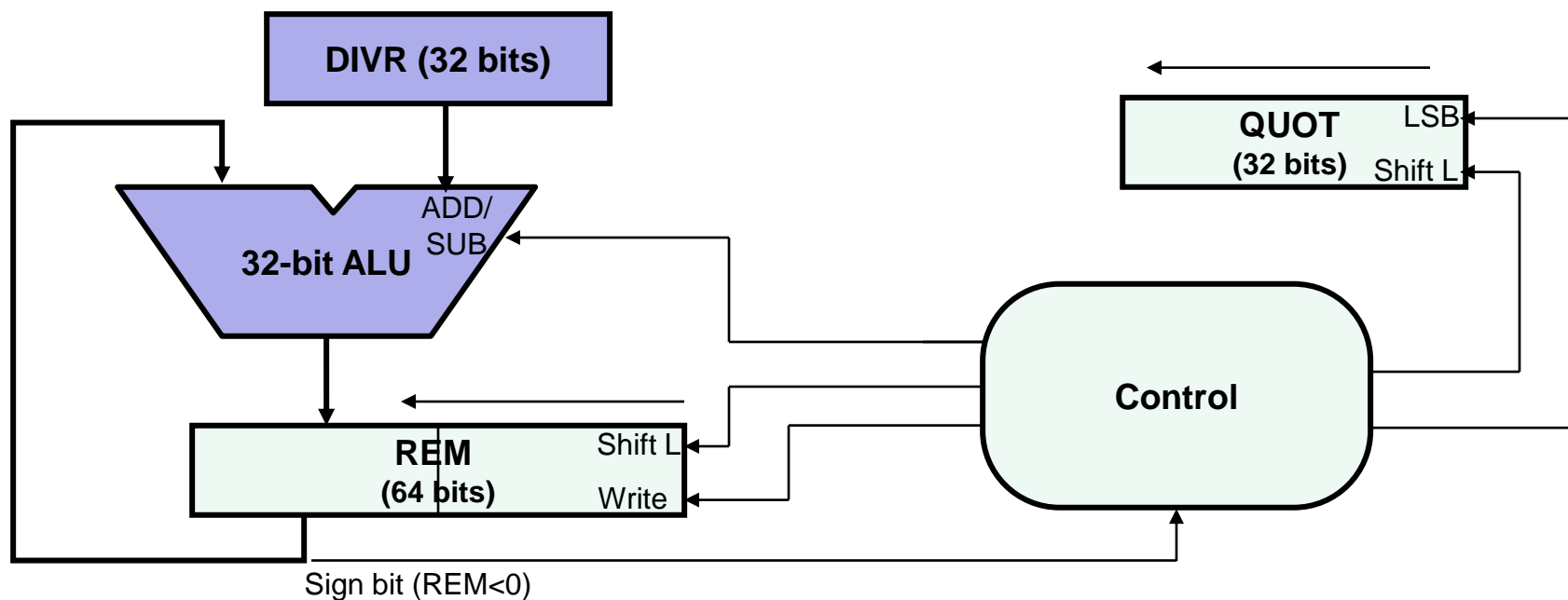- ▶ **Divisor Holds Still**
- ▶ **Dividend/Remainder Shifts Left**
- ▶ **End Result: Remainder in upper half of register**




Divide Hardware - 3rd Version

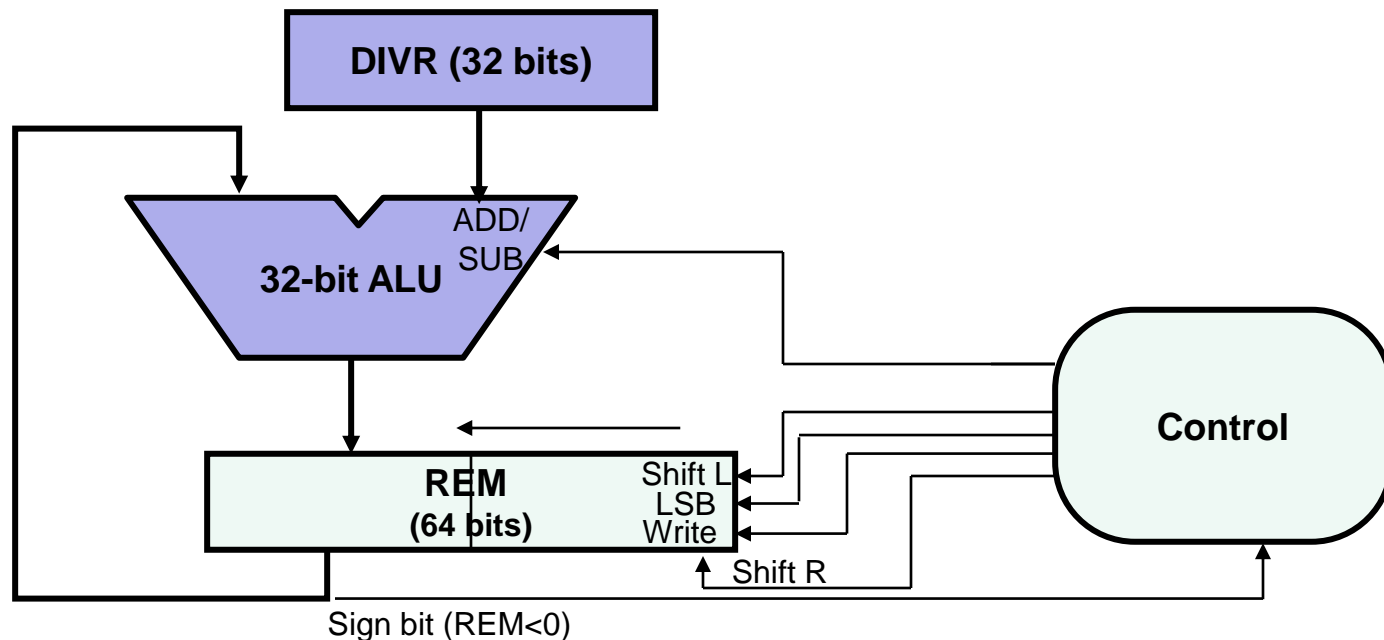- Combine quotient with remainder register



Divide Algorithm - 3rd Version

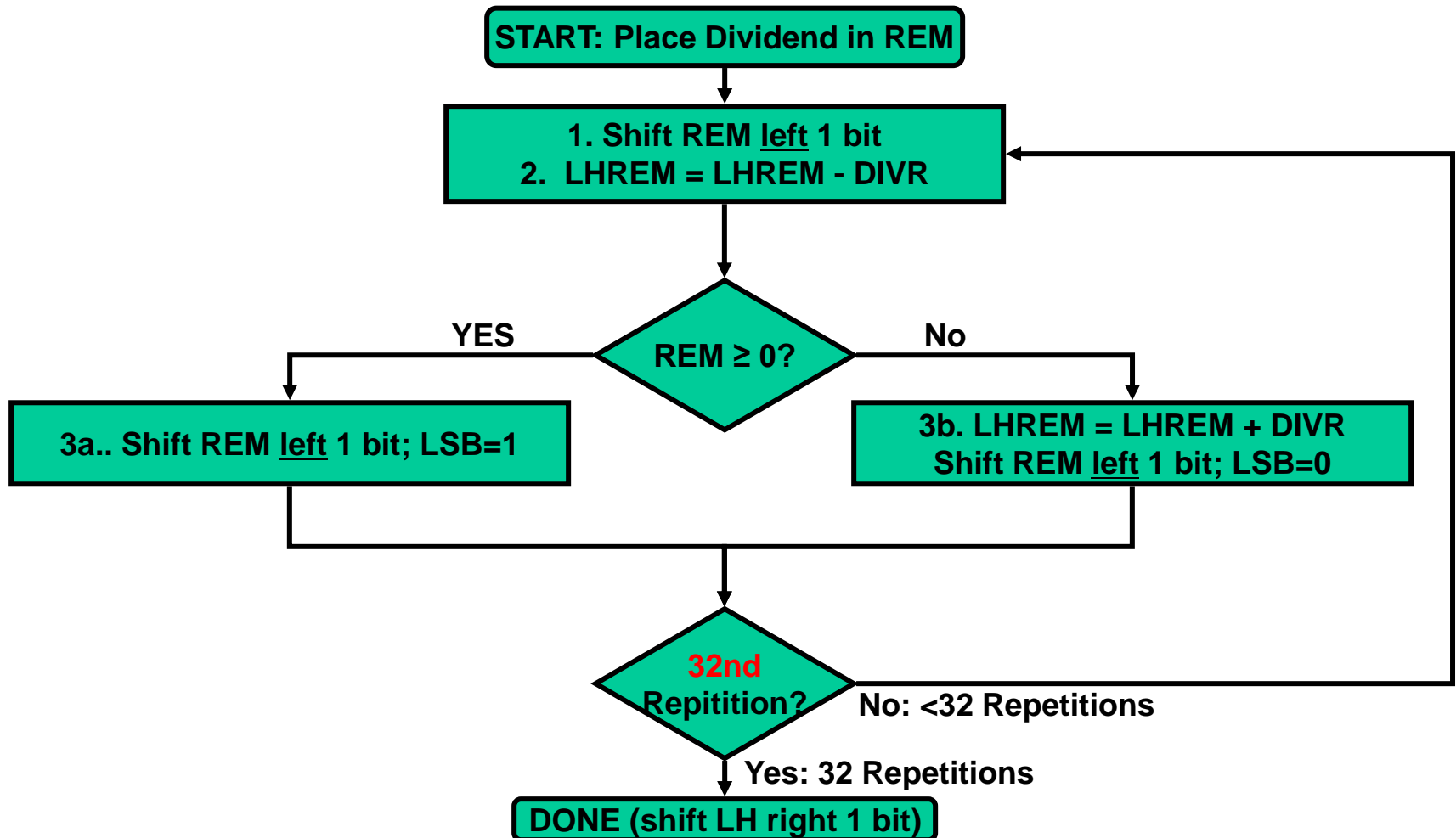

Dividing Signed Numbers

- ▶ Check sign of divisor, dividend
- ▶ Negate quotient if signs of operands are opposite
- ▶ Make remainder sign match dividend (if nonzero)

Outline - Multiplication and Division

- ▶ **Multiplication**
 - ▶ Review: Shift & Add Multiplication
 - ▶ Review: Booth's Algorithm
 - ▶ Combinational Multiplication
 - ▶ MIPS Multiplication Instructions
- ▶ **Division**
 - ▶ Division Algorithms
 - ▶ **MIPS Division Instructions** ◀
- ▶ **Summary**

Divide Instructions in MIPS

▶ Divide Instructions

- ▶ `div $s2, $s3` # $\text{Lo} = \$s2 / \$s3$; $\text{Hi} = \$s2 \% \$s3$
- ▶ `divu $s2, $s3` # $\text{Lo} = \$s2 / \$s3$; $\text{Hi} = \$s2 \% \$s3$

▶ Results in Lo, Hi registers

- ▶ **Hi**: remainder
- ▶ **Lo**: quotient

▶ Divide pseudoinstructions

- ▶ `div $s3, $s2, $s1` # $\$s3 = \$s2 / \$s1$
- ▶ `divu $s3, $s2, $s1`

`div $s3, $s2, $s1`



`div $s2, $s1`

`mflo $s3`

▶ Software must check for overflow, divide-by-zero

Outline - Multiplication and Division

- ▶ **Multiplication**
 - ▶ Review: Shift & Add Multiplication
 - ▶ Review: Booth's Algorithm
 - ▶ Combinational Multiplication
 - ▶ MIPS Multiplication Instructions
- ▶ **Division**
 - ▶ Division Algorithms
 - ▶ MIPS Division Instructions
- ▶ **Summary** ◀

Summary - Multiplication and Division

- ▶ **Multiplication**
 - ▶ Sequential multipliers - efficient but slow
 - ▶ Combinational multipliers - fast but expensive
- ▶ **Division is more complex and problematic**
 - ▶ What about **divide by zero**?
 - ▶ Restore step needed to undo unwanted subtractions
 - ~~Nonrestoring division: combine restore w/ next subtract~~
- ▶ **Take a Computer Arithmetic course for more details**
- ▶ **Coming Up: Floating Point**